



Dr. Phung Thi Kieu Ha

Electronic Circuits and Applications

Lesson 3. FET small-signal amplifier

Learning Contents

1. Introduction of FET devices
2. FET biasing
3. FET small-signal amplifier
4. Comparison

Learning Goals

1. Be able to perform a dc analysis of JFET and MOSFET networks.
2. Become acquainted with the small-signal ac model for a JFET and MOSFET.
3. Be able to perform a small-signal ac analysis of a variety of JFET and MOSFET configurations.
4. Be able to analyze cascaded configurations with FETs and/or BJT amplifiers.

1. Introduction

1.1. FET characteristics & classifications

1.2. JFET

1.3. DMOS

1.4. EMOS

1. Introduction

1.1. FET characteristics & classification

- Very large input impedance, $nM\Omega$ - $n100M\Omega$
- To control by voltage
- Low power consumption
- Low noise suitable for small signal source
- Less impact by temperature
- Small size, production technology allow to integrate very large number of devices
- Good as a switch

1. Introduction


1.1. FET characteristics & classification

Classification

- JFET-Junction Field Effect Transistor
 - ✓ N-channel
 - ✓ P-channel
- MOSFET-Metal Oxide Semiconductor FET
 - ✓ Depletion-type - DMOS
 - N and P channel
 - ✓ Enhancement-type - EMOS
 - N and P channel



1. Introduction

1.2. JFET structure & operation

 

1. Introduction


1.2. JFET structure & operation

  


$V_{GS} = 0$, V_{DS} increases, I_D increases

1. Introduction

1.2. JFET structure & operation

 

 
$V_{GS} < 0$, $V_{DS} > 0$,
the saturation level of
 I_D decrease



$V_{GS} = V_P$ (pinch-off voltage),
 $I_D = 0$



1. Introduction

1.2. JFET structure & operation

 

1. Introduction


1.3. D-MOSFET structure & operation

  

N-channel depletion DMOS

1. Introduction

1.3. D-MOSFET structure & operation

 


Transfer characteristic follows Shockley equation:

$$I_D = I_{DSS}(1 - V_{GS}/V_P)^2$$

Note: DMOS can operate at $V_{GS} > 0$, $I_D > I_{DSS}$, enhancement mode


1. Introduction

1.4. E-MOSFET structure & operation

 


N-channel EMOS

$$V_{GS} > 0, V_{DS} > 0$$

 

1. Introduction

1.4. E-MOSFET structure & operation

 

Different transfer characteristics



$$I_D = k(V_{GS} - V_T)^2 \text{ in which } V_T > 0 \text{ (N channel)}$$

Note: $V_{GS} < V_T$, $I_D = 0$



1. Introduction

Summary



JFET

  

DMOS

  

EMOS

  

2. FET biasing

2.1. Fix bias configuration

2.2. Self-bias conf.

2.3. Voltage-divider conf.

2.4. Voltage-feedback conf.

2. FET biasing

The relationship of current & voltage when FET is in
“amplifier” mode

For all type of FET:

$$I_G = 0A$$

$$I_D = I_S$$

JFET & DMOS:

$$I_D = I_{DSS}(1 - V_{GS}/V_P)^2$$



EMOS:

$$I_D = k(V_{GS} - V_T)^2$$

Non-linear relationship of V_{GS} and I_D

2. FET biasing

2.1. Fix bias circuit

  

$$I_G = 0, V_S = 0$$



$$V_{GS} = V_G = -V_{GG},$$

V_{GS} is fixed by a DC voltage source V_{GG}

$$I_D = I_{DSS}(1 - V_{GS}/V_p)^2$$

2. FET biasing

2.1. Fix bias circuit

  

Load line equation

$$V_{GS} = -V_{GG}$$


2. FET biasing

2.1. Fix bias circuit

In reality, leakage current I_{GSS} increases with temperature that it can not be neglected

Operating point movement

$$V_{GS} = V_{GG} + I_{GSS} * R_G$$

 

2. FET biasing

2.2. Fix bias circuit

$V_{GG} = -1V$ and $R_G = 1\text{ M}\Omega$.

$I_{GSS} = 10\text{ nA}$ at room temperature 25°C
and double when temperature increases
 10°C .

V_{GS} at temp of 125°C ?

Solution


At 25°C , $I_{GSS} \times R_G = 10^{-9} \times 10^6 = 1\text{ mV}$,
neglected since $V_{GG} = -1V$.

At 125°C , I_{GSS} increase 2^{10} ($\approx 10^3$), then

$$I_{GSS} = 10^3 \times 1\text{ nA} = 1\text{ }\mu\text{A}$$

$$I_{GSS} \times R_G = 1V$$


 
$$V_{GS} = 0V \text{ and } I_D = I_{DSS}$$



Moved Q is far from the pre-designed configuration at room temperature

2. FET biasing

2.2. Self-bias circuit

  



$$I_G = 0 \Rightarrow V_G = 0V \Rightarrow$$

$$V_{GS} = -I_S R_S$$

$$I_D = I_{DSS} (1 - V_{GS}/V_p)^2$$

2. FET biasing

2.2. Self-bias circuit

  


Load line equation

$$V_{GS} = -I_S R_S$$

2. FET biasing


2.2. Self-bias circuit

 

- What is the difference from Fix-base?
- Why is it called “self-bias”?
- What is the role of R_S ?
- Can we neglect R_G ?
- How is the temperature stability?

2. FET biasing

2.3. Voltage-divider bias for JFET

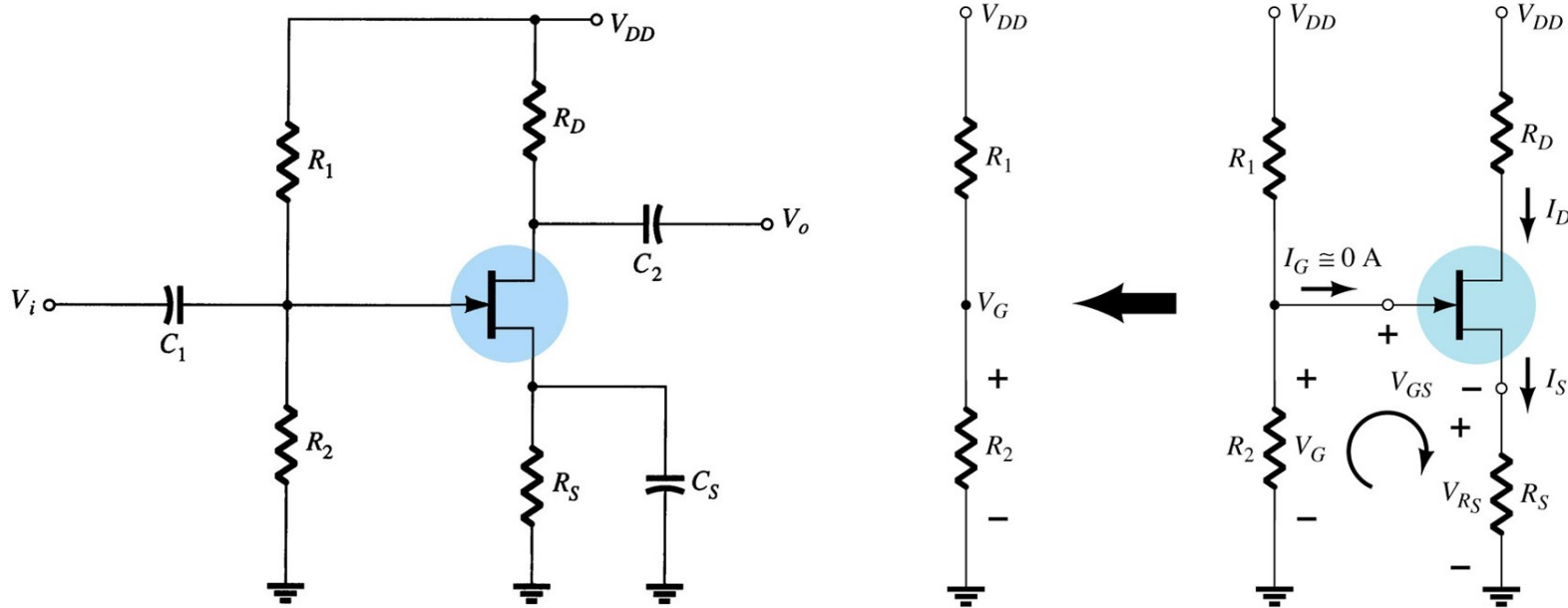



$$I_G = 0, \text{ then } V_G = V_{DD} R_2 / (R_1 + R_2)$$

$$V_{GS} = V_G - I_D R_S$$

$$I_D = I_{DSS} (1 - V_{GS} / V_P)^2$$


2. FET biasing

2.3. Voltage-divider bias for JFET

  

2. FET biasing

2.3. Voltage-divider bias for DMOS

 

$$V_G = V_{DD} * 10\text{M}\Omega / (110\text{M}\Omega + 10\text{M}\Omega)$$

Load line equation

$$V_{GS} = V_G - I_S * 0.75\text{K}\Omega \quad (1)$$



DMOS characteristic:

$$I_D = I_{DSS} (1 - V_{GS}/V_P)^2 \quad (2)$$

Note: V_{GS} can be positive

2. FET biasing

2.3. Voltage-divider bias for DMOS

 
 


DMOS: $I_D = I_{DSS}(1 - V_{GS}/V_P)^2$

V_{GS} can be positive

2. FET biasing

2.3. Voltage-divider bias for EMOS

  



EMOS characteristics:

$$I_D = k(V_{GS} - V_T)^2$$

$$k = I_{D(on)} / (V_{GS(on)} - V_T)^2$$

2. FET biasing

2.4. Voltage-feedback bias for EMOS

  

$$I_G = 0 \Rightarrow V_G = V_D$$



$$V_{GS} = V_{DS} = V_{DD} - R_D I_D$$

$$I_D = k(V_{GS} - V_T)^2$$

$$k = I_{Don} / (V_{GSon} - V_T)^2$$

2. FET biasing

2.4. Voltage-feedback bias for EMOS

  

Can this configuration be used to bias JFET?

3. FET small-signal amplifier

3.1. Equivalent circuit model

3.2. Common-Gate circuit


3.3. Common-Source circuit

3.4. Common-Drain circuit

3.5. Common-Source configuration with EMOS

3. FET Small-signal amplifier

3.1. FET equivalent model

 

An open-circuit between G and S as
very large input impedance (n100-
n1000 M Ω)


A voltage-controlled current source

A trans-conductance factor g_m –

An output impedance r_d

3. FET small-signal amplifier

3.1. FET equivalent model

 


$$g_m = \Delta I_D / \Delta V_{GS} = d(I_D(V_{GS}))$$

Show the speed of the variation of I_D in the variation of V_{GS}

3. FET small-signal amplifier

3.1. FET equivalent model

 


g_m depends on the operating point

Approximately determine the g_m at the operating point

3. FET small-signal amplifier

3.1. FET equivalent model

 



Similar to the model of JFET

Note on the possible value of g_m

3. FET small-signal amplifier

3.1. FET equivalent model

EMOSFET

  

3. FET small-signal amplifier

3.1. FET equivalent model

Trans-conductance factor of
JFET/DMOS

Shockley equation for
transfer characteristics

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$

=> trans-conductance

$$g_m = \frac{2I_{DSS}}{|V_P|} \left[1 - \frac{V_{GS}}{V_P} \right]$$

3. FET small-signal amplifier

3.1. FET equivalent model

Transfer characteristics
equation

$$I_D = k(V_{GS} - V_{GS(Th)})^2$$

Trans-conductance factor of
EMOS



$$g_m = 2k(V_{GS_Q} - V_{GS(Th)})$$

in which k is determined

$$k = \frac{I_{D(on)}}{(V_{GS(on)} - V_{GS(Th)})^2}$$

3. FET small-signal amplifier

3.2. Common-Gate configuration

  

3. FET small-signal amplifier

3.2. Common-Gate configuration


$$Z_i = R_s // [(r_d + R_D) / (1 + g_m r_d)] \quad \approx R_s // (1/g_m) \text{ when } r_d > 10R_D$$

$$Z_o = r_d // R_D \quad \approx R_D \quad \text{when } r_d > 10R_D$$

$$A_v = [g_m R_D + (R_D / r_d)] / [1 + R_D / r_d] \approx g_m R_D \quad \text{when } r_d > 10R_D$$

3. FET small-signal amplifier

3.3. Common-Source configuration

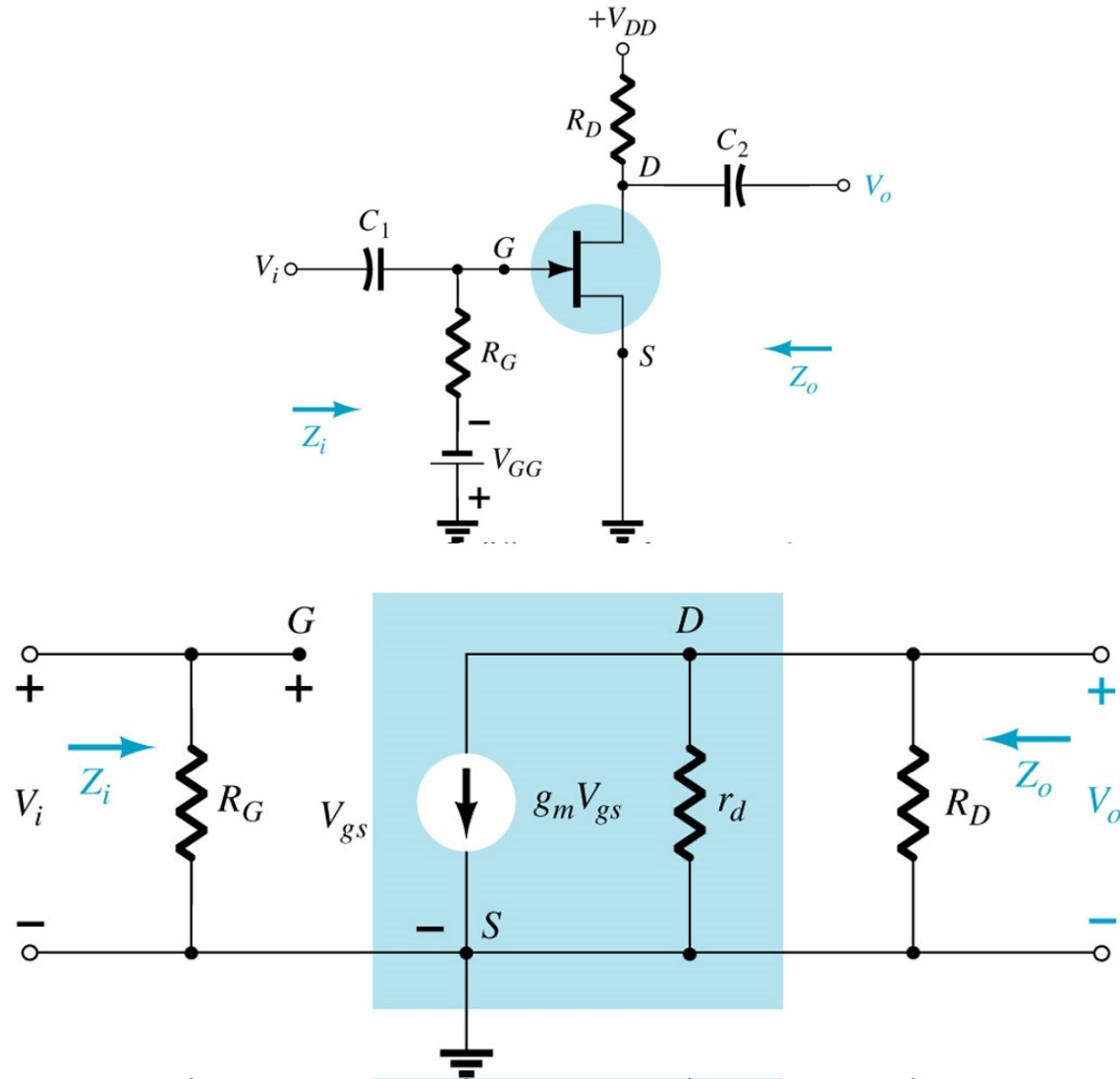

3. FET small-signal amplifier

3.3. Common-Source configuration

$$Z_i = R_G$$


$$Z_o = r_d // R_D \approx R_D \quad \text{when } r_d > 10R_D$$

$$A_v = -g_m(r_d // R_D) \approx -g_m R_D \quad \text{when } r_d > 10R_D$$

V_i & V_o are in reversed phase

3. FET small-signal amplifier

3.4. Common-Drain configuration

 

3. FET small-signal amplifier

3.4. Common-Drain configuration

$$Z_i = R_G$$

$$Z_o = r_d // R_S // (1/g_m) \approx R_S // (1/g_m) \quad \text{when } r_d > 10R_S$$

$$A_v = -g_m(r_d // R_S) / [1 + g_m(r_d // R_S)]$$
$$\approx g_m R_S / [1 + g_m R_S]$$


$$\approx 1$$

$$\text{when } r_d > 10R_S$$

$$\text{when } g_m R_S \gg 1$$

3. FET small-signal amplifier

 3.5. Common-Source configuration with EMOS



3. FET small-signal amplifier

3.5. Common-Source configuration with EMOS

$$Z_i = (R_F + r_d // R_D) / [1 + g_m (r_d // R_D)]$$
$$\approx R_F / (1 + g_m R_D) \quad \text{when } r_d > 10R_D, R_F \gg r_d // R_D$$

$$Z_o = R_F // r_d // R_D$$
$$\approx R_D \quad \text{when } r_d > 10R_D, R_F \gg r_d // R_D$$

$$A_V = g_m R_F // r_d // R_D$$
$$\approx g_m R_D \quad \text{when } r_d > 10R_D, R_F \gg r_d // R_D$$

Summary

1. **Transfer characteristic** equation shows a **nonlinear** relationship between the gate-to-source voltage and the drain current of a FET device.
2. A **very large input impedance** between the gate and the source allows that the gate current is zero.
3. The **trans-conductance g_m** is determined by the ratio of the change in drain current associated with a particular change in gate-to-source voltage in the region of interest.
4. The **magnitude of voltage gain** of FET networks, except the common-gate configuration, are typically between 2-20 times, normally lower than the BJT networks.
5. The **input impedance** for most FET configurations is quite high, except that it is quite low for the common-gate configuration.

Next lesson guide...

Lesson 4: Effect of Load & Source Resistance

Reference

*Electronics devices and Circuits theory – Robert Boylestad, Louis Nashelsky,
Prentice Hall, 11th edition*

Electronic principles – Albert Paul Malvino